

Lab 2 Power Field Effect Transistors

Driving an LED

1. Assemble the circuit in Fig. 1
2. Assume that $R_{DS} = 5\Omega$ and that $V_{LED} = 2.25V$
 3. Calculate I_D _____
 4. Measure V_{LED} _____
 5. Measure I_D _____
 6. Using the value of V_{LED} from step 4, calculate a new value for the current limiting resistor R1 so that I_D is approximately 20mA.
 7. Rebuild the circuit using the new value of R1 and measure I_D _____
 8. How close is the measured value of I_D to the new specification of 20mA?

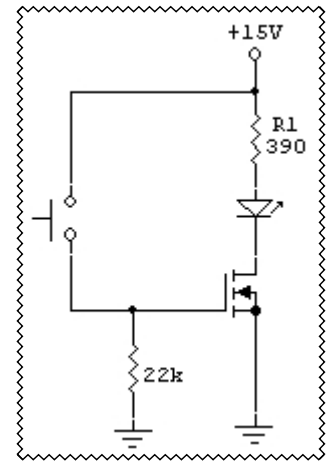


Fig. 1

D. C. Motor Control

1. Assemble the circuit in Fig. 2 using a D.C. motor.
2. Vary the potentiometer so that speed of the motor varies.
3. Measure V_{GS} for the following conditions:
 4. Motor turns on: $V_{GS} =$ _____
 5. Motor speed maximum: $V_{GS} =$ _____
 6. Motor turns off: $V_{GS} =$ _____
4. Reverse the polarity of the D.C. Motor and repeat steps 4, 5, 6.
 - Motor turns on: $V_{GS} =$ _____
 - Motor speed maximum: $V_{GS} =$ _____
 - Motor turns off: $V_{GS} =$ _____

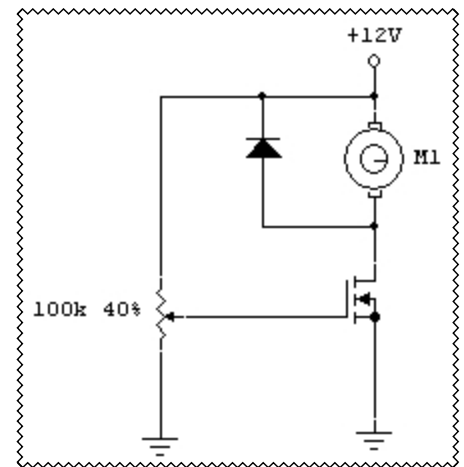


Fig. 2

5. Is there a difference in the operation of the motor when the polarity was reversed?

Soft Turn-On (Soft Start)

1. Assemble the circuit in Fig. 3.

2. Calculate the time constant of the resistor-capacitor network connected to the gate. $\tau = RC =$ _____

3. Connect a voltmeter across the capacitor.

4. Close the switch and observe the voltmeter as the voltage rises.

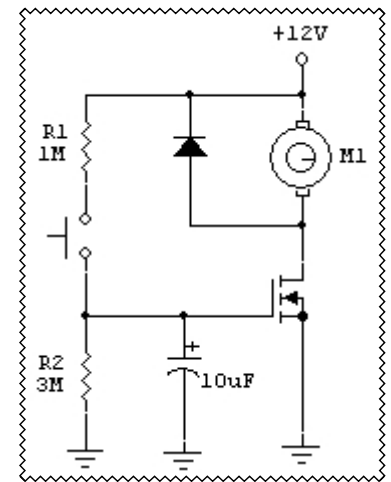


Fig. 3

5. Use a watch and note the time when the motor starts. $t =$ _____

6. Open the switch and once again observe the voltmeter and note the time for the motor to stop. $t =$ _____

7. Replace the capacitor with a $22\mu F$ capacitor. Repeat steps 2 to 6. What is the effect of a larger capacitor on the operation of the circuit?