

Lab 2 Part 3 Bridge Rectifier

1. Assemble the circuit if Fig. 1:

2. Measure secondary voltage with voltmeter in A.C.: $V_{SEC} =$ _____

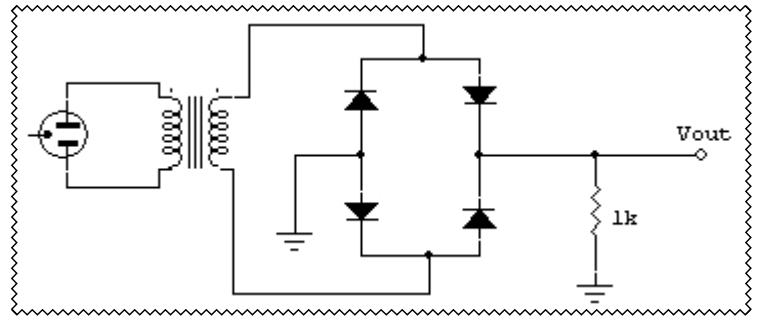


Fig. 1

3. Calculate peak voltage: $V_p =$ _____

4. Calculate load voltage: $V_L =$ _____

5. Calculate D.C. voltage: $V_{DC} =$ _____

6. Measure D.C. voltage with voltmeter in D.C.: $V_{DC} =$ _____

7. Connect channel 1 of the oscilloscope to V_{OUT} and sketch the output in Fig. 2. Indicate peak voltage and the period of the waveform.

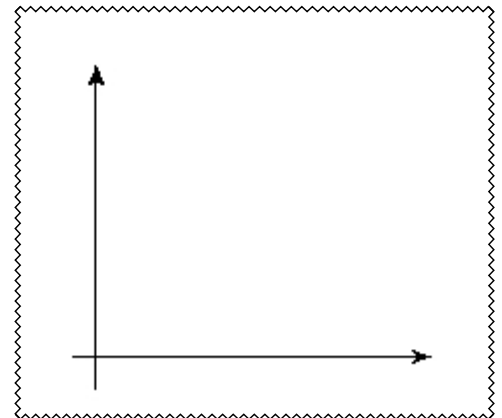


Fig. 2

8. Modify the circuit as in Fig. 3:

9. Measure V_{OUT} with the voltmeter in D. C.
 $V_{DC} =$ _____

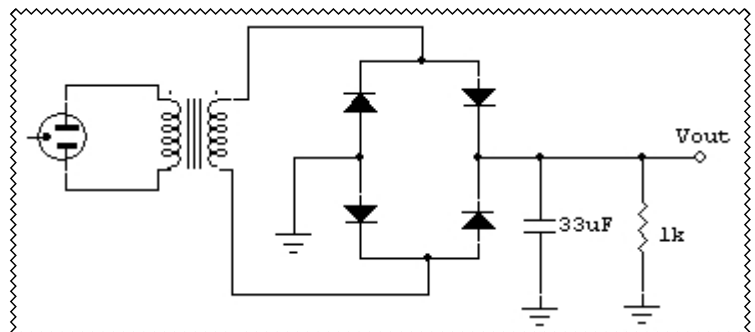


Fig.3

10. Calculate load current: $I_L =$ _____

11. Measure load current with the ammeter in D.C.: $I_L =$ _____

12. Connect channel 1 of the oscilloscope to V_{OUT} and sketch ripple voltage in Fig. 4. Indicate value of peak to peak ripple voltage and the ripple frequency.

13. What is the effect of adding a capacitor to the circuit?

14. Modify the circuit in Fig.3 by increasing the capacitor to $470\mu F$:

15. Measure load voltage: $V_L =$ _____

Measure load current: $I_L =$ _____

16. Again connect the oscilloscope to V_{OUT} and observe the new value of ripple voltage: $V_{RIPPLE} =$ _____

17. What is the effect of increasing capacitance in the circuit?

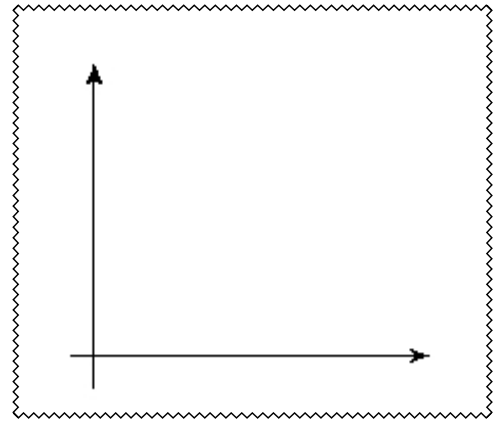


Fig. 4