

Lab 2 Part 1 and Part 2
Rectifier Circuits

Part 1. Half-wave rectifier

1. Assemble the circuit in Fig. 1

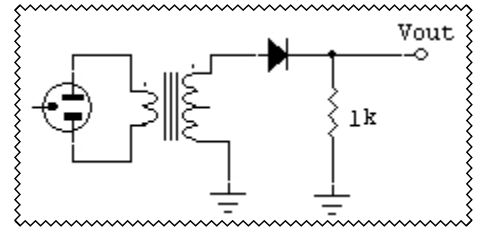


Fig. 1

2. Measure V_{SEC} with the voltmeter in A.C.: $V_{SEC} =$ _____

3. Calculate V_P : $V_P =$ _____

4. Calculate V_L : $V_L =$ _____

5. Calculate V_{DC} : $V_{DC} =$ _____

6. Measure V_{OUT} with the voltmeter in D.C.: $V_{DC} =$ _____

7. How do the calculated and measured values of V_{DC} compare?

8. Connect channel 1 of the oscilloscope to V_{OUT} . Sketch the output in Fig. 2 and indicate V_P and the period of the waveform.

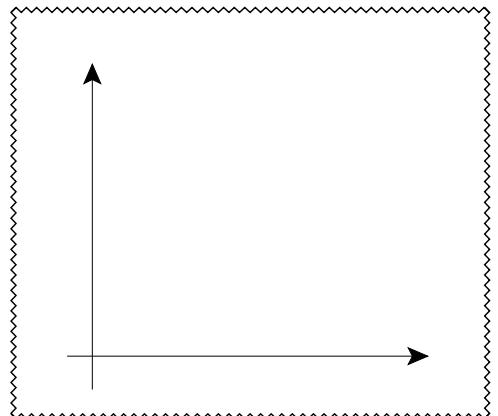


Fig.2

Part 2 Full Wave Rectifier

1. Assemble the circuit in Fig. 3

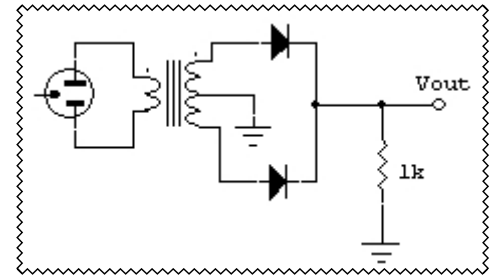


Fig. 3

2. Measure V_{SEC} with the voltmeter in A.C.:

$$V_{SEC} = \underline{\hspace{2cm}}$$

3. Calculate V_{CT} : $V_{CT} = \underline{\hspace{2cm}}$

Measure V_{CT} : $V_{CT} = \underline{\hspace{2cm}}$

Do these voltages match?

4. Calculate V_p : $V_p = \underline{\hspace{2cm}}$

5. Calculate V_L : $V_L = \underline{\hspace{2cm}}$

6. Calculate V_{DC} : $V_{DC} = \underline{\hspace{2cm}}$

7. Measure V_{OUT} with the voltmeter in D.C.:

$$V_{DC} = \underline{\hspace{2cm}}$$

8. Connect to oscilloscope to V_{OUT} . Sketch the output in Fig. 4 and indicate V_p and the period of the waveform.

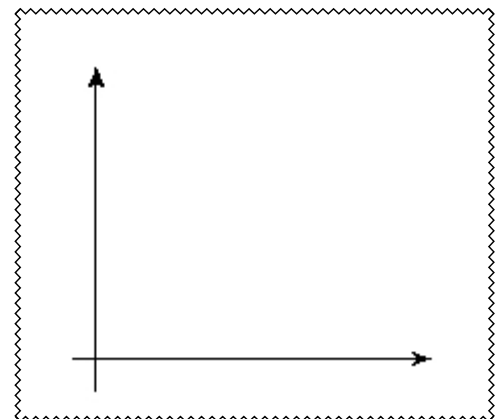


Fig. 4

9. What are the differences between the half-wave and full-wave rectifier circuits?