

Lab 5
Transistor Introduction

Transistor Operating Regions

Cut-Off

1. Assemble the circuit in Fig. 1:
2. Measure the following values:

$$I_B = \underline{\hspace{2cm}}$$

$$I_C = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

3. What controls the collector current?

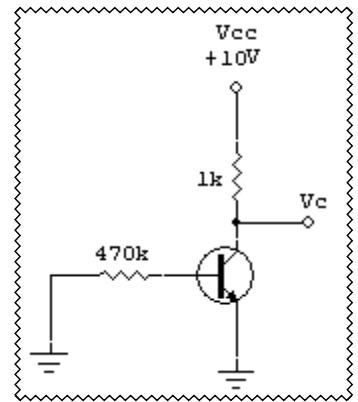


Fig.1

Saturation

4. Assemble the circuit in Fig. 2; assume that $\beta = 200$:
5. Calculate the following values:

$$I_B = \underline{\hspace{2cm}}$$

$$I_C = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

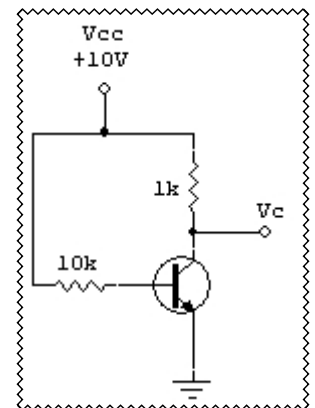


Fig. 2

6. Are there illogical values in Step 5? If so, is the transistor saturated?
7. Calculate collector current:

$$I_C = \underline{\hspace{2cm}}$$

8. Measure the following values:

$$I_C = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$I_B = \underline{\hspace{2cm}}$$

(Hint: must be very low)

(The current will be very low)

Active Transistor

9. Assemble the circuit in Fig. 3; assume the $\beta = 200$

10. Calculate the following values:

$$I_B = \underline{\hspace{2cm}}$$

$$I_C = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

11. Is the transistor active?

12. Measure the following values:

$$V_{BE} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$I_B = \underline{\hspace{2cm}}$$

$$I_C = \underline{\hspace{2cm}}$$

$$\beta = \underline{\hspace{2cm}}$$

13. What causes the variations between the calculated values and measure values in step 12?

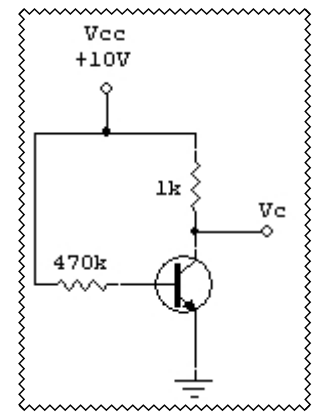


Fig. 3