

Lab 6
Transistor Switch, Current Source

Transistor Switch

1. Assemble the circuit in Fig. 1:
2. Assume that the circuit in Fig. 1 is in saturation due to the 10 to 1 relation between R_B and R_C . Then what should be the value of V_C ?

$$V_C = \underline{\hspace{2cm}}$$

3. Again assuming saturation, calculate I_C .

$$I_C = \underline{\hspace{2cm}}$$

4. Measure the following values:

$$I_C = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{LED} = \underline{\hspace{2cm}}$$

(Hint: the voltage drop across the LED.)

5. Select a new value for R_C so that the current through the LED is 30mA. Use the value of V_{LED} from step 4 in your calculations.

6. Modify the circuit and measure the current through the LED:

$$I_{LED} = \underline{\hspace{2cm}}$$

(Hint: same as collector current, I_C)

Current Source

7. Assemble the circuit in Fig. 2:
8. Calculate the following:

$$V_B = \underline{\hspace{2cm}}$$

$$V_E = \underline{\hspace{2cm}}$$

$$I_C = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

(To determine if transistor is active)

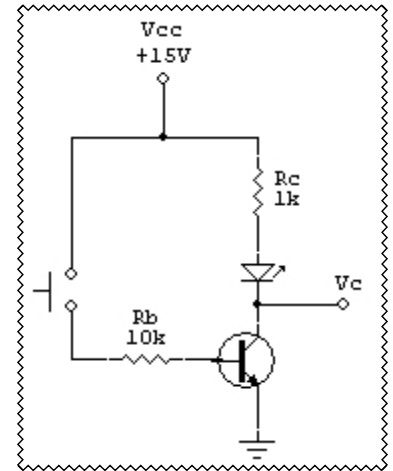


Fig. 1

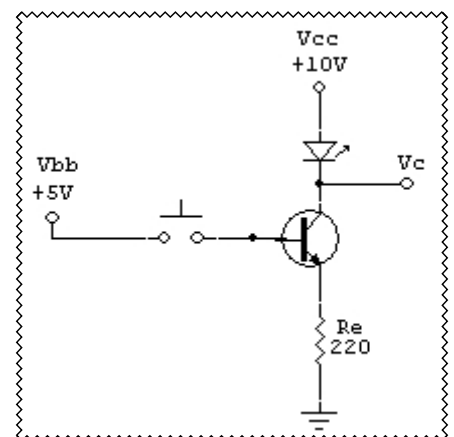


Fig. 2

9. Measure the following values:

$$V_B = \underline{\hspace{2cm}}$$

$$V_E = \underline{\hspace{2cm}}$$

$$I_C = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

10. Select a new value for R_E so the LED current is 30mA. (Use the value of V_{LED} from step 4 in your calculations.)

11. Modify the circuit and once again measure the current through the LED.

$$I_{LED} = \underline{\hspace{2cm}}$$

12. In both circuits how do the calculated and measured values compare?