

Lab 7
NPN Transistor Bias, Q-point

1. Assemble the circuit in Fig. 1:
2. Calculate the following values:

$$V_B = \underline{\hspace{2cm}}$$

$$V_E = \underline{\hspace{2cm}}$$

$$I_E \doteq I_C = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

Is the transistor active?

What is the Q-point?

3. Additional calculations:

Cut-off: $V_{CE} = \underline{\hspace{2cm}}$

Saturation: $I_C = \underline{\hspace{2cm}}$

4. Using the values from the previous calculations, draw the load line and plot the Q-point in Fig. 2:

5. Measure the values calculated in step 2 and comment on how well the values match.

$$V_B = \underline{\hspace{2cm}}$$

$$V_E = \underline{\hspace{2cm}}$$

$$I_E \doteq I_C = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

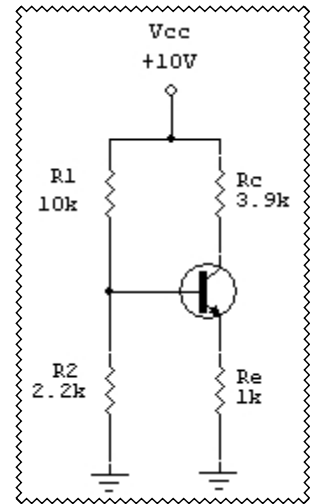


Fig.1

(This step is optional in some books.)

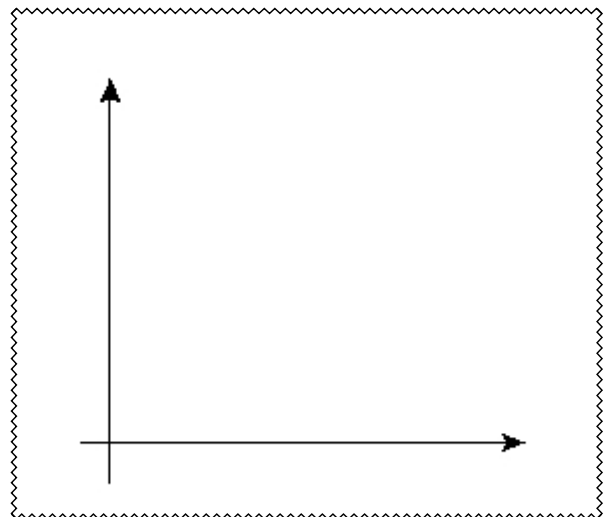


Fig. 2