

Lab 10 Class A Amplifier

1. Assemble the circuit in Fig.1:

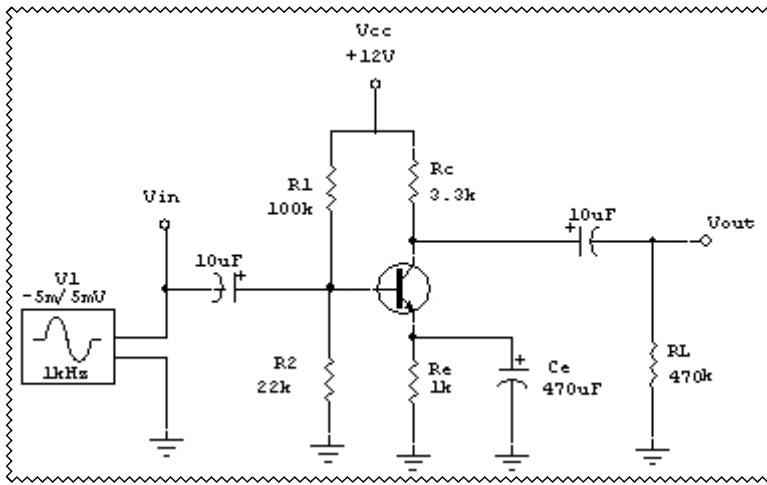


Fig 1

$$r'_{be} = \frac{25mV}{I_{CEQ}} =$$

AC resistance of the collector (little r'_c)

$$r'_c = R_c \parallel R_L =$$

Gain

$$A_v = \frac{r'}{r'_{be}} =$$

2. Calculate and measure the following values:

$$V_B = \underline{\hspace{2cm}}$$

$$V_E = \underline{\hspace{2cm}}$$

$$I_E \doteq I_C = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

$$\text{Q-point: } \underline{\hspace{2cm}}$$

3. Find the DC load line:

$$I_{SAT} = \underline{\hspace{2cm}}$$

$$V_{CEoff} = \underline{\hspace{2cm}}$$

4. AC values:

AC resistance of base-emitter junction (little r'_{be})

5. AC load line:

AC saturation:

$$i_{SAT} = I_{CEQ} + \frac{V_{CEQ}}{r'_c} =$$

6. Output values:

$$\text{Maximum peak: } MP = I_{CEQ}(r'_c) =$$

$$\text{Maximum peak to peak: } MPP = 2(MP) =$$

$$\text{Output power to load: } P_{OUT} = \frac{MPP^2}{8R_L} =$$

7. Efficiency calculations:

Current in biasing network:

$$I_{BIAS} = \frac{V_{CC}}{R_1 + R_2} =$$

Total biasing current and collector current:

$$I_{DC} = I_{BIAS} + I_{CEQ} =$$

Total power to stage (P_{IN}): $P_{DC} = V_{CC} I_{DC} =$

Efficiency: $\eta = \frac{P_{OUT}}{P_{IN}} (100\%) =$

8. Draw the DC and AC load lines in Fig. 2:

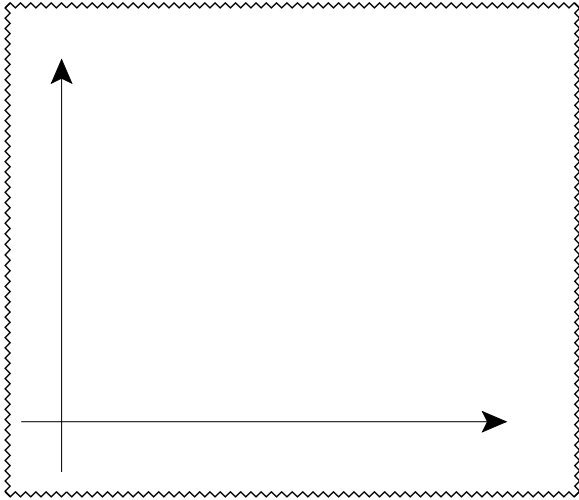


Fig. 2

9. Connect Channel 1 of the oscilloscope to V_{in} and Channel 2 to V_{out} . Sketch the signals Fig.3 and Fig. 4. 4. Do the calculated and measure values match? Is the output signal distorted?

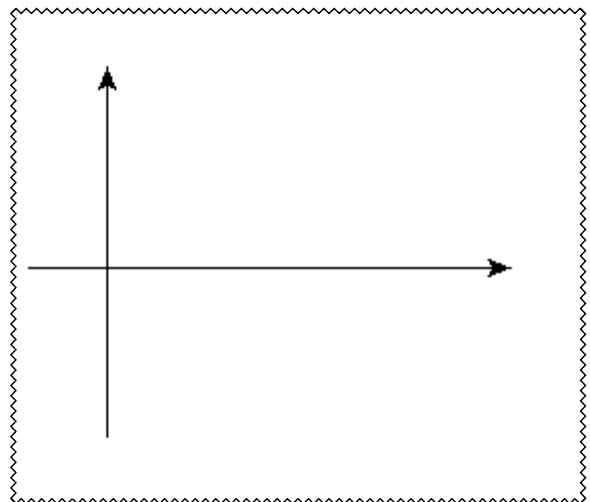
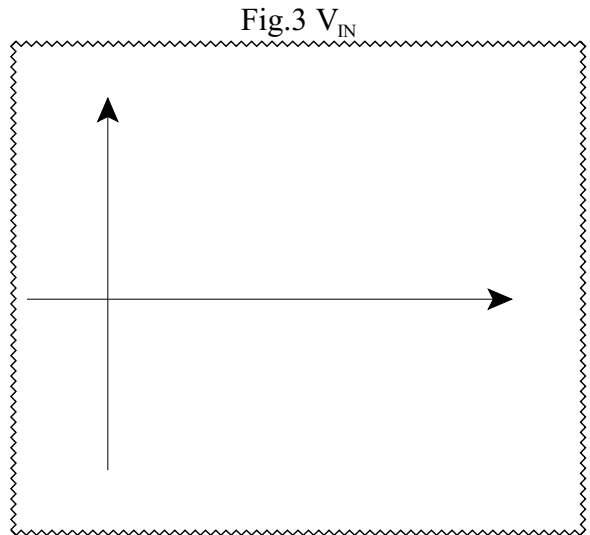


Fig. 4 V_{OUT}