

Lab 9 Common Emitter Amplifier

1. Assemble the circuit in Fig. 1:

2. Calculate the following DC values:

$$V_B = \underline{\hspace{2cm}}$$

$$V_E = \underline{\hspace{2cm}}$$

$$I_E \doteq I_C = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

Is the transistor active?

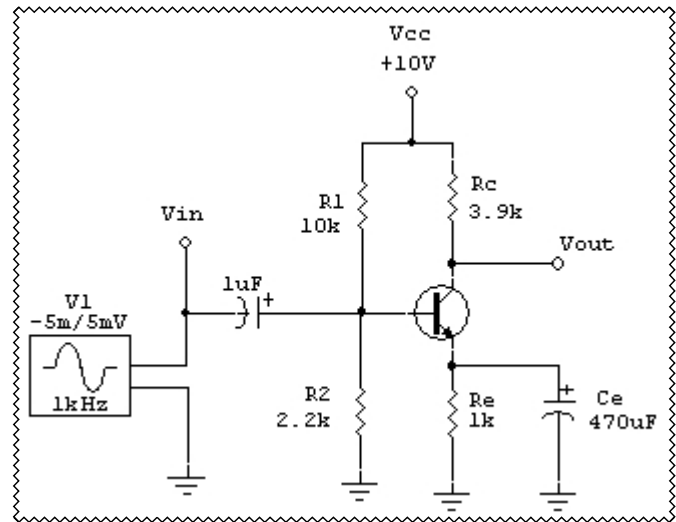


Fig. 1

3. Calculate the following AC values:

(AC resistance of the base-emitter junction) $r'_{be} = \underline{\hspace{2cm}}$

Gain: $A_v = \underline{\hspace{2cm}}$

4. Measure the values that were calculated in step 2:

$$V_B = \underline{\hspace{2cm}}$$

$$V_E = \underline{\hspace{2cm}}$$

$$I_E \doteq I_C = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$V_{CE} = \underline{\hspace{2cm}}$$

$$V_{BC} = \underline{\hspace{2cm}}$$

5. Connect channel 1 of the oscilloscope to V_{IN} and channel 2 to V_{OUT} . (Notice that the input signal is a sine wave of $10mV_{pp}$ at 1kHz.)

Measure the gain: $A_V = \underline{\hspace{2cm}}$

6. Sketch the input and output waveforms. (Notice that V_{OUT} should be "riding" on V_C which is a DC value.)
What is the relationship between the two waveforms?
How do the calculated and measured values compare?

Fig. 2 V_{IN}

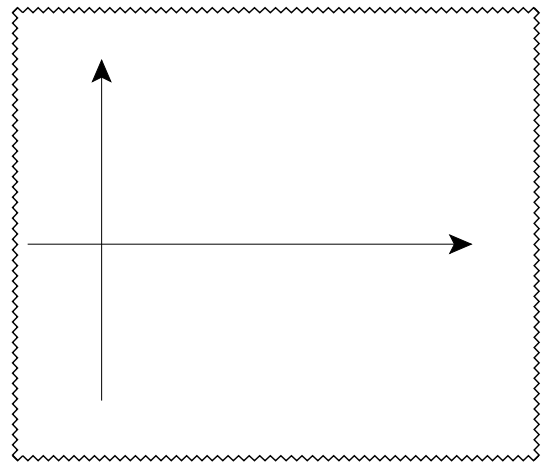
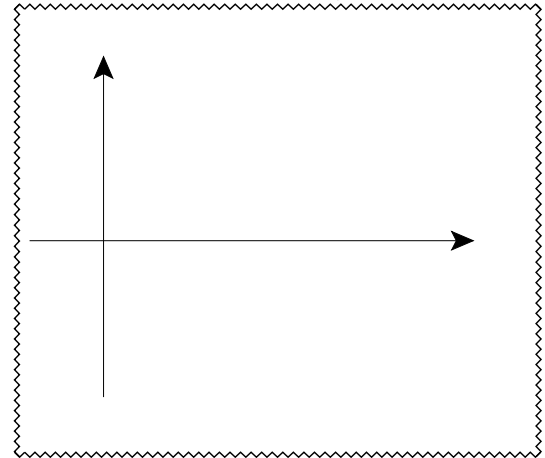


Fig. 3 V_{OUT}