

Lab 12 Class C Amplifiers

1. Assemble the following circuit in Fig. 1
2. Place channel 1 of the oscilloscope at the input to the capacitor to see V_{IN} . Then move channel 1 to the other side of the capacitor or V_B which is the base of the transistor to see the effect of clamping. (The oscilloscope coupling should be DC.)
3. Place channel 2 of the oscilloscope to V_{out} .
4. Sketch to input and the output signals in Fig. 2.
5. Is the transistor on or off?

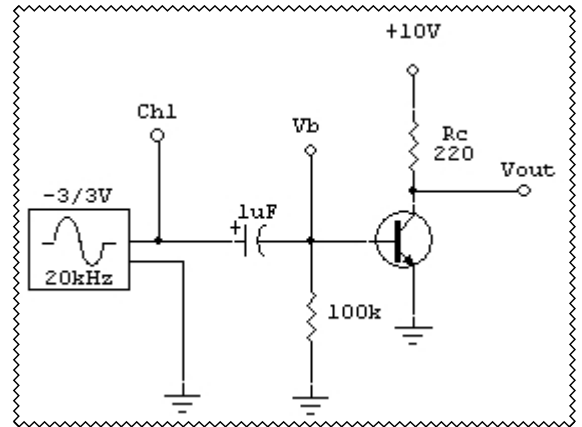


Fig 1

Fig. 2 V_{in}

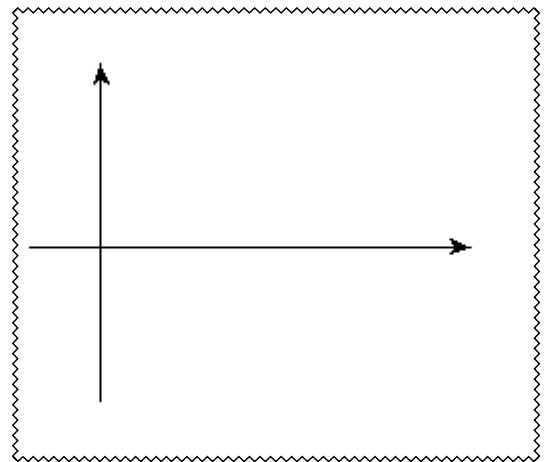
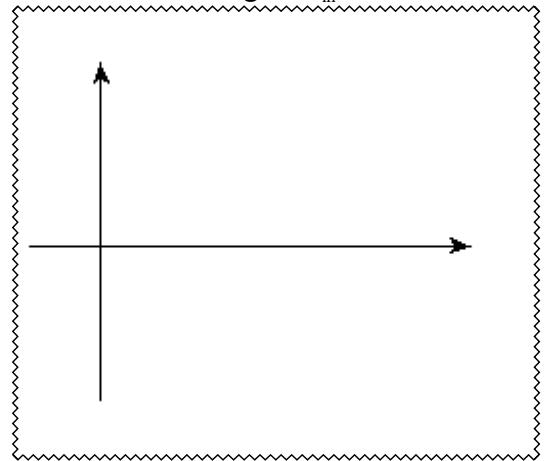


Fig. 2 V_{OUT}

6. Assemble the circuit in Fig. 3:
7. Calculate the resonant frequency:
8. Calculate the bandwidth:

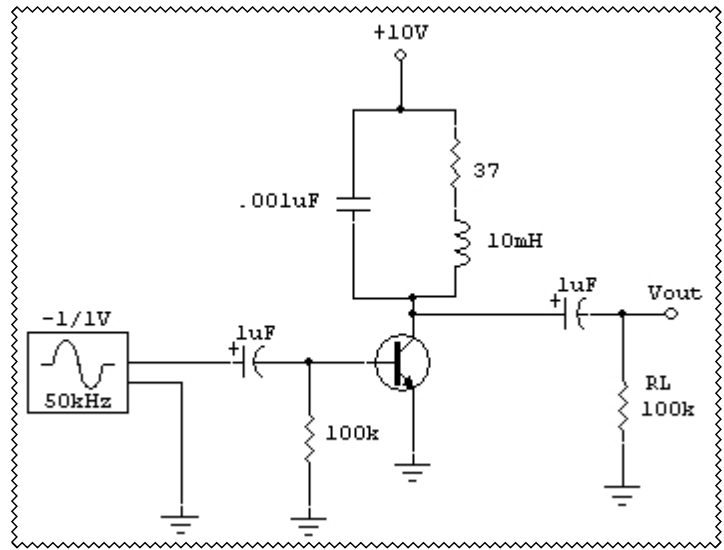


Fig. 3

9. Adjust the signal generator for a maximum output. (Let this be the “center frequency”.)
10. Increase the frequency until the output drops to .707 of the maximum output. (Let this be the high corner frequency F_H .)
11. Return to the center frequency and then lower the frequency until the output drops to .707 of the maximum output. (Let this be the low corner frequency F_L .)
12. Create a Bode plot in Fig. 4 and indicate the corner frequencies, maximum output and bandwidth.

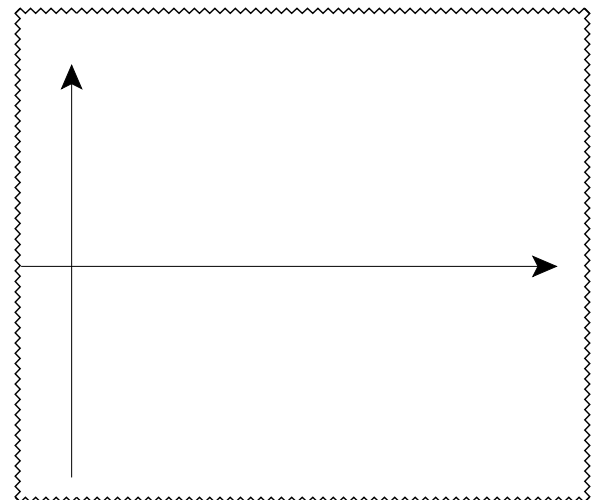


Fig. 4