

Lab 10 (Rev. 1)
Part 1
Positive Feedback Schmitt Trigger Oscillator

1. Assemble the circuit if Fig.1:

2. What are the two possible outputs for this circuit?

$$V_{OUT} = \underline{\hspace{2cm}}$$

What are the two possible thresholds for this circuits?

$$V_{THR} = \underline{\hspace{2cm}}$$

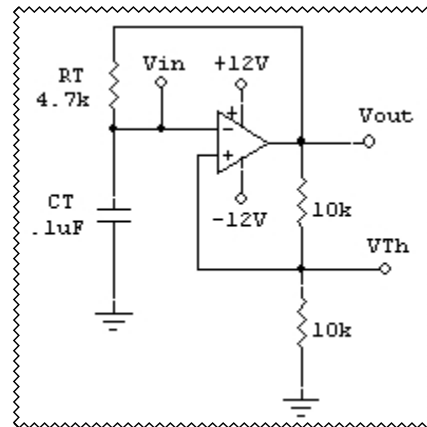


Fig. 1

3. Calculate the frequency of oscillation:

$$F_R = \frac{1}{2RC} =$$

4. Connect channel 1 of the oscilloscope to V_{IN} and channel 2 to V_{OUT} .

5. Sketch the two waveforms in Fig. 2; indicate the output levels and the thresholds levels.

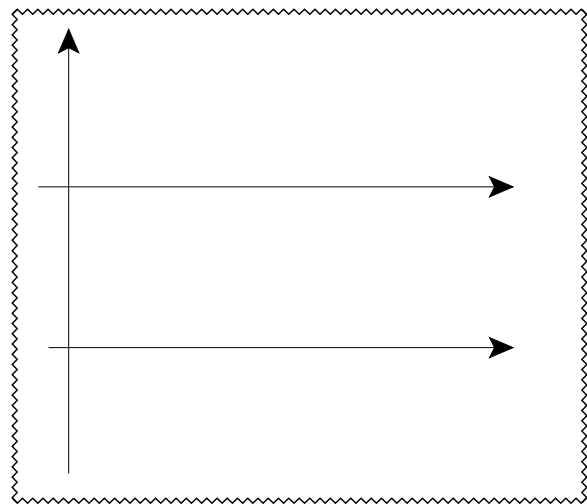


Fig. 2

6. Measure the frequency of oscillation; does the measured frequency match the calculated frequency?

7. Modify the circuit as in Fig. 3:

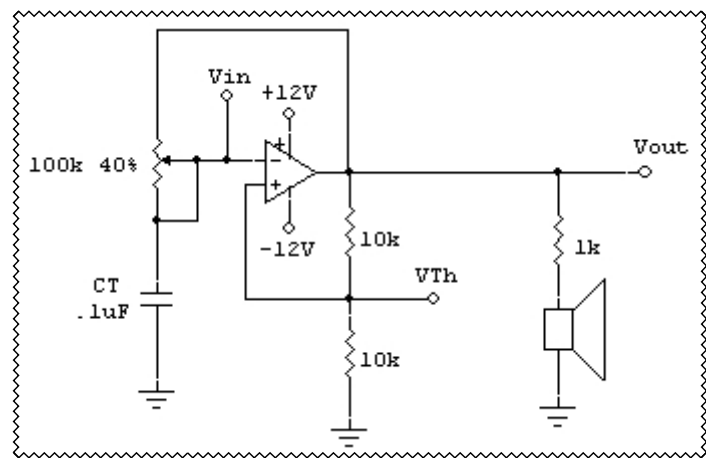


Fig 3

8. Operate the circuit; what is the lowest frequency that this oscillator will produce?

$F_L =$ _____

9. What is the highest frequency that is produced?

$F_H =$ _____

Lab 10 Part 2

Schmitt Trigger with “Deadband”

1. Assemble the circuit in Fig. 4. Place the voltmeter at V_{TH} in order to measure the upper and lower trip points.

2. Rotate the potentiometer so that the forward biased LED is on. Measure the value of “upper trip point” when this LED is on:

UTP = _____

3. Rotate the potentiometer in the opposite direction so that the reverse biased LED is on and measure the “lower trip point” LTP = _____

4. The results of the measurements in step 2 and 3 is that there are two trip points, upper and lower. Also there are only two possible outputs, positive and negative saturation. Place the voltmeter at V_{OUT} and measure the two output voltages (by rotating the potentiometer to create forward and reverse outputs:)

$+V_{SAT}$ = _____

$-V_{SAT}$ = _____

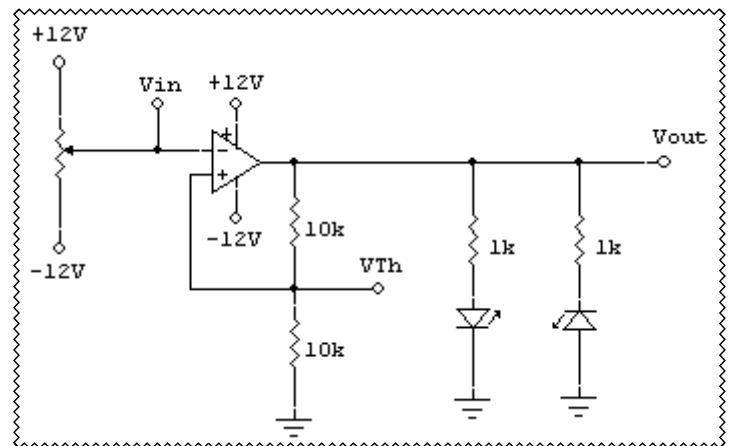


Fig. 4

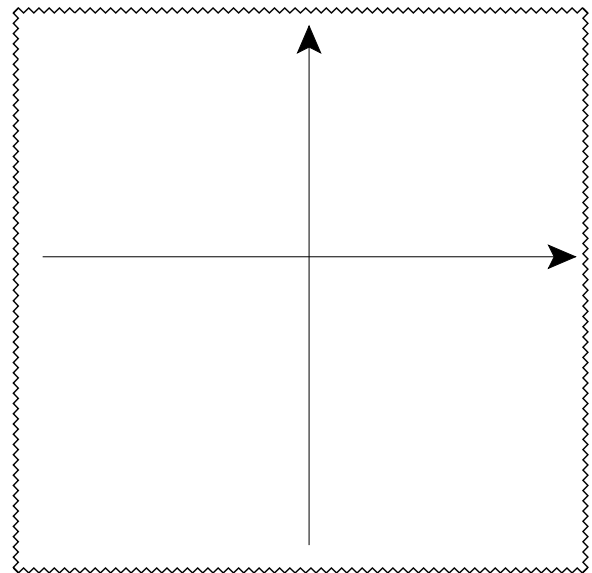


Fig. 5

5. Plot the two trip points and the two saturations in Fig. 5:

6. The “deadband” is the distance between the two trip points; what is this deadband in volts? V = _____

7. Move the potentiometer in both directions. Measure the value of V_{IN} . If V_{IN} is above the “upper trip point”, the output should saturate negative. But if V_{IN} is below the “lower trip point”, the output should saturate positive; is this true?

8. What happens to the output inside the “deadband”?