

ET 386L  
Lab Quiz 2

Name:

1. Observe the following circuit:
2. Create a program that will cause the circuit to produce a pitch of 3kHz. Show all your calculations.
3. Make appropriate comments after every line. Draw the wave that will be produced by the program and indicate the period and frequency.

